 




PAMANTASAN NG LUNGSOD NG MAYNILA
(University of the City of Manila)
Intramuros, Manila

Microprocessor Lab

Laboratory Activity No. 2
Arduino and Tinkercad Interface



Score

Submitted by:
Bitara, Jan Vincent S.
< Saturday 10:30am – 1:00pm > / < CPE 0412-1.1 >

Date Submitted
30-09-2023

Submitted to:
Engr. Maria Rizette H. Sayo

I. Objectives

This laboratory activity aims to implement the principles and techniques of hardware programming using Arduino through:

- creating an Arduino programming and circuit diagram.

II. Method/s

- Perform a task problem given in the presentation.
- Write a code and perform an Arduino circuit diagram of a ring counter that display eight (8) LEDs starting from left.

III. Results

TinkerCad

Exercise 1: Write a code that does a ring counter display for eight (8) LEDs starting from left.

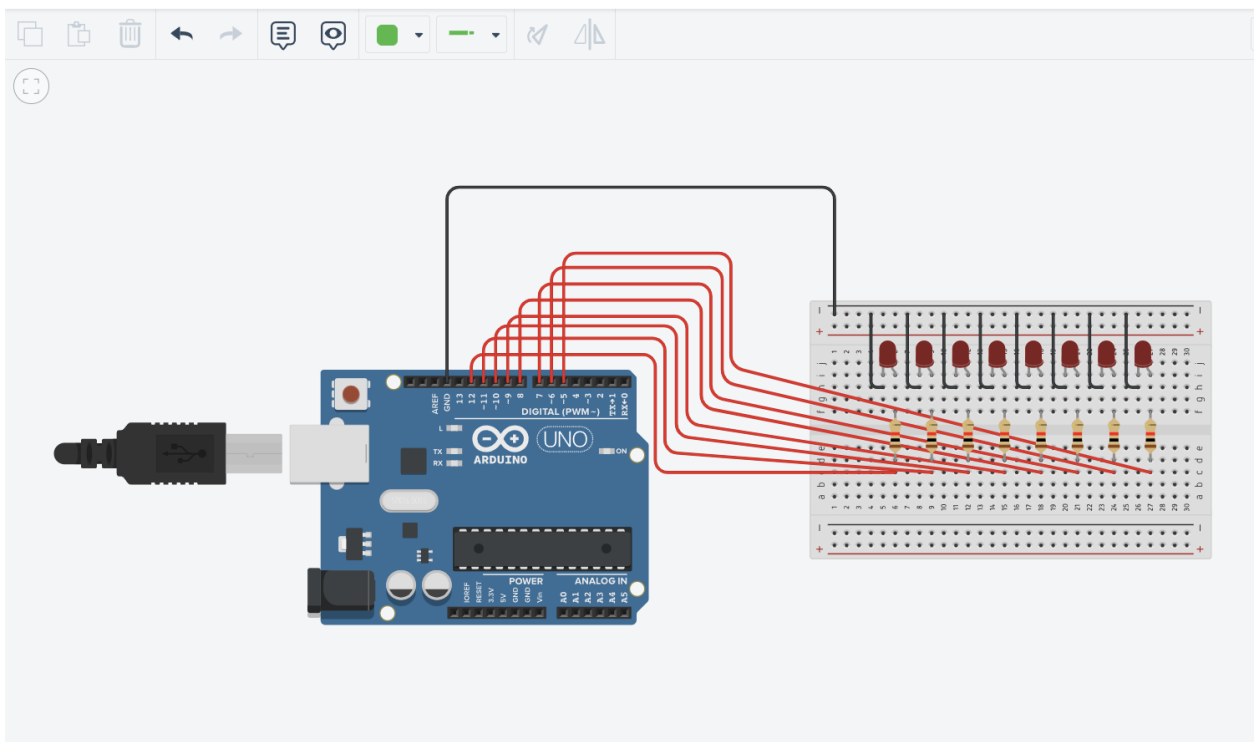


Figure No.1 Ring Counter Display Circuit Diagram


Components Used

1. 8 LEDs
2. Resistor
3. Breadboard

CODE:

```
1 // C++ code
2 //
3 /*
4  * Ring counter display for eight (8) LEDs starting from left.
5  */
6
7 void setup()
8 {
9     Serial.begin(9600);
10    pinMode(5, OUTPUT);
11    pinMode(6, OUTPUT);
12    pinMode(7, OUTPUT);
13    pinMode(8, OUTPUT);
14    pinMode(9, OUTPUT);
15    pinMode(10, OUTPUT);
16    pinMode(11, OUTPUT);
17    pinMode(12, OUTPUT);
18 }
19
20 void loop()
21 {
22     digitalWrite(12, HIGH);
23     delay(500);
24     Serial.println("The LED1 is HIGH");
25     digitalWrite(12, LOW);
26     delay(500);
27     Serial.println("The LED1 is LOW");
28
29     digitalWrite(11, HIGH);
30     delay(500);
31     Serial.println("The LED2 is HIGH");
32     digitalWrite(11, LOW);
33     delay(500);
34     Serial.println("The LED2 is LOW");
35
36     digitalWrite(10, HIGH);
37     delay(500);
38     Serial.println("The LED3 is HIGH");
39     digitalWrite(10, LOW);
40     delay(500);
41     Serial.println("The LED3 is LOW");
42
43     digitalWrite(9, HIGH);
44     delay(500);
45     Serial.println("The LED4 is HIGH");
46     digitalWrite(9, LOW);
47     delay(500);
48     Serial.println("The LED4 is LOW");
49
50     digitalWrite(8, HIGH);
51     delay(500);
52     Serial.println("The LED5 is HIGH");
53     digitalWrite(8, LOW);
54     delay(500);
55     Serial.println("The LED5 is LOW");
56
57     digitalWrite(7, HIGH);
58     delay(500);
59     Serial.println("The LED6 is HIGH");
60     digitalWrite(7, LOW);
61     delay(500);
62     Serial.println("The LED6 is LOW");
63
64     digitalWrite(6, HIGH);
65     delay(500);
66     Serial.println("The LED7 is HIGH");
67     digitalWrite(6, LOW);
68     delay(500);
69     Serial.println("The LED7 is LOW");
70
71     digitalWrite(5, HIGH);
72     delay(500);
73     Serial.println("The LED8 is HIGH");
74     digitalWrite(5, LOW);
75     delay(500);
76     Serial.println("The LED8 is LOW");
77
78 }
```

IV. Conclusion

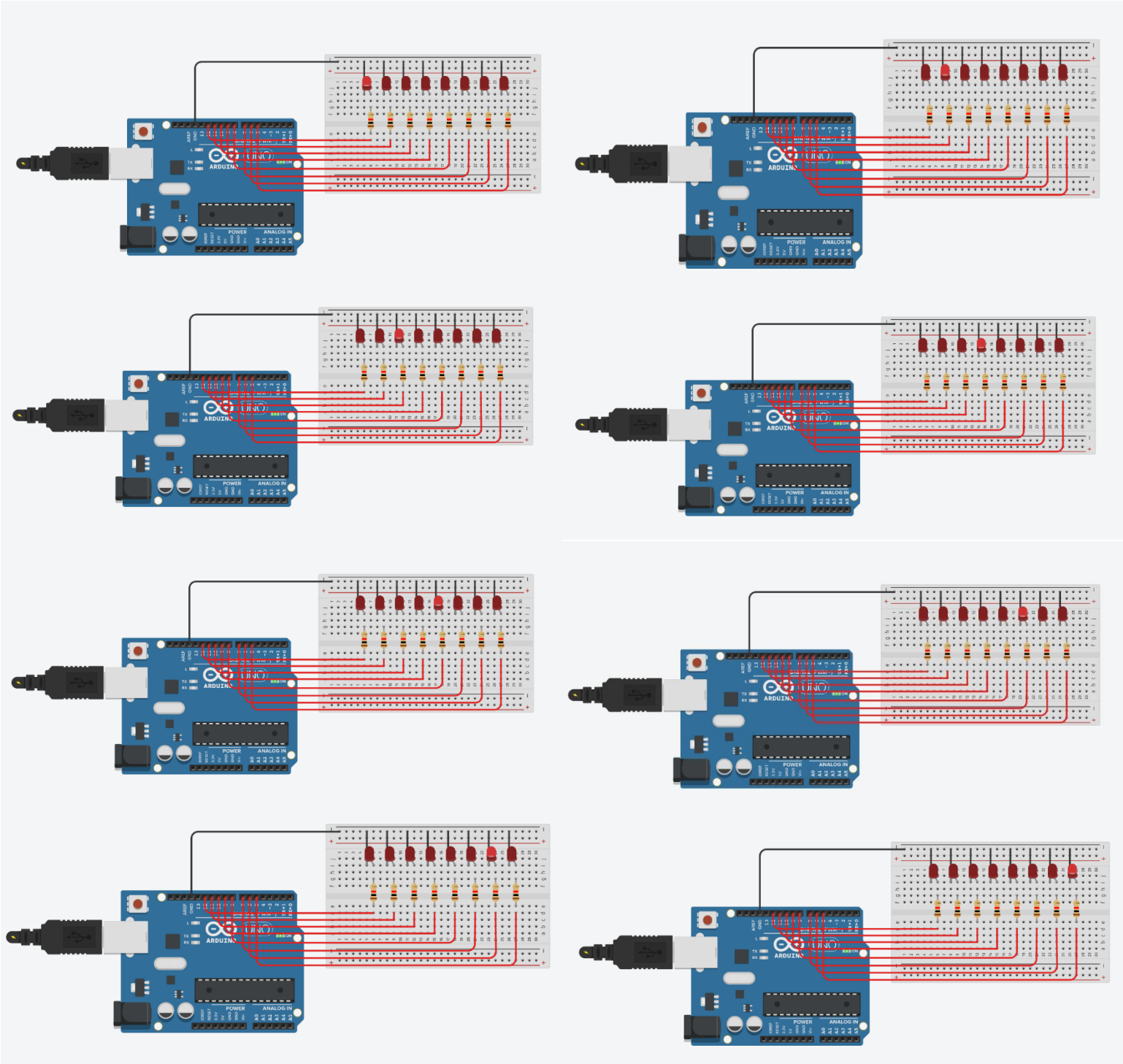

The 8-LED ring counter display is a simple but effective way to demonstrate the concept of a ring counter. The circuit is relatively easy to build and requires only a few basic components: an Arduino board, a breadboard, jumper wires, and 8 LEDs. The circuit works by sequentially turning on and off the LEDs in a ring. The Arduino board controls the switching of the LEDs using a simple program. The program uses a counter to keep track of which LED should be turned on next.

References

[1] D.J.D. Sayo. “University of the City of Manila Computer Engineering Department Honor Code,” PLM-CpE Departmental Policies, 2020.

<This is in a separate page>